



# ***Technology Mapping The Directed Acyclic Graph-Covering Problem and The Tree-Covering Problem***

***Presented by:***

***Rashed Hassan Siam***

***Class Roll: FH-2343***

***Registration No: 2022-518-433***

***Department of Computer Science  
and Engineering***

***University of Dhaka***

***Presented to:***

***Professor Dr. Hafiz Md. Hasan Babu***

***Department of Computer Science  
and Engineering***


***University of Dhaka***

# Contents

- *Technology Mapping and its Approaches*
- *Dos and Don'ts of Technology Mapping*
- *Directed Acyclic Graph*
- *Prerequisites and Goals of the DAG-Covering Problem*
- *Choice of Base Functions*
- *Creating the Subject and Pattern Graphs*
- *The DAG-Covering Problem Complexity*
- *Alternative Approach: The Tree-Covering Problem*
- *Splitting Subject Graph into Trees*
- *The Tree Mapping Procedure*
- *Pattern Matching*
- *Tree Covering*
- *Advantages and Limitations of The Tree-Covering Problem*

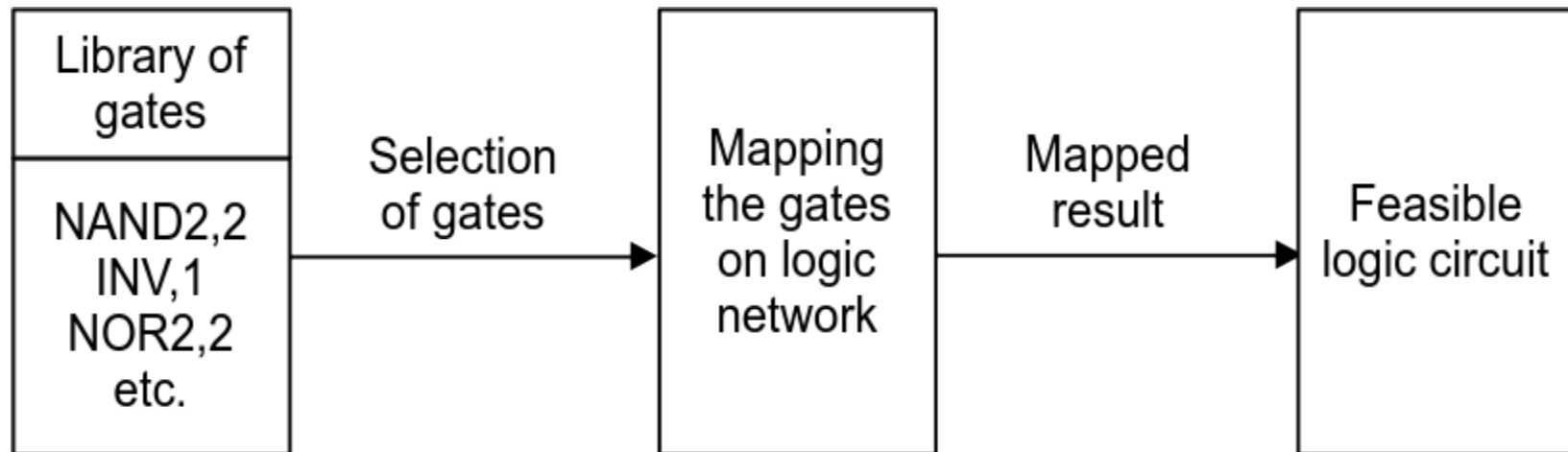
# Technology Mapping

- Helps to implement a logic circuit.
- Performs the final gate selection from a particular library.
- The library is also known as the Technology Library.
  - ↳ Consists of several gates (NAND2,2; NOR2,2; INV,1 etc.).


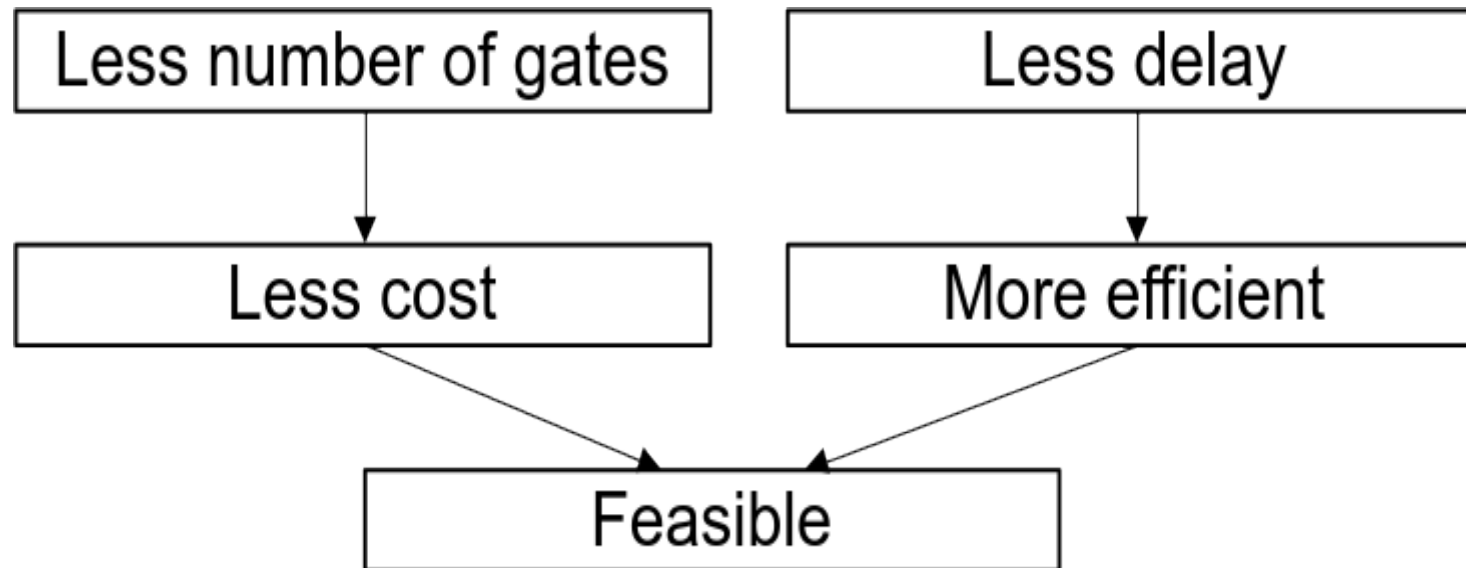
# Feasible Circuits

- Optimal with respect to area.
  - Least number of nodes/gates.
- Satisfies a maximum critical-path delay.
  - The longest path of the circuit from input to output.
  - Should be within a specified threshold.



# ***Dos and Don'ts of Technology Mapping***

## Technology Mapping



```
graph LR; A[Technology Mapping] --> B[Doesn't change the structure of the circuit radically.]; A --> C[Doesn't reduce the number of levels of logic.]; A --> D[Chooses the fastest gates along the critical path.]; A --> E[Uses the most area-efficient combination of gates.];
```


➤ Doesn't change the structure of the circuit radically.

➤ Doesn't reduce the number of levels of logic.

➤ Chooses the fastest gates along the critical path.

➤ Uses the most area-efficient combination of gates.


# ***Technology Mapping Approaches***

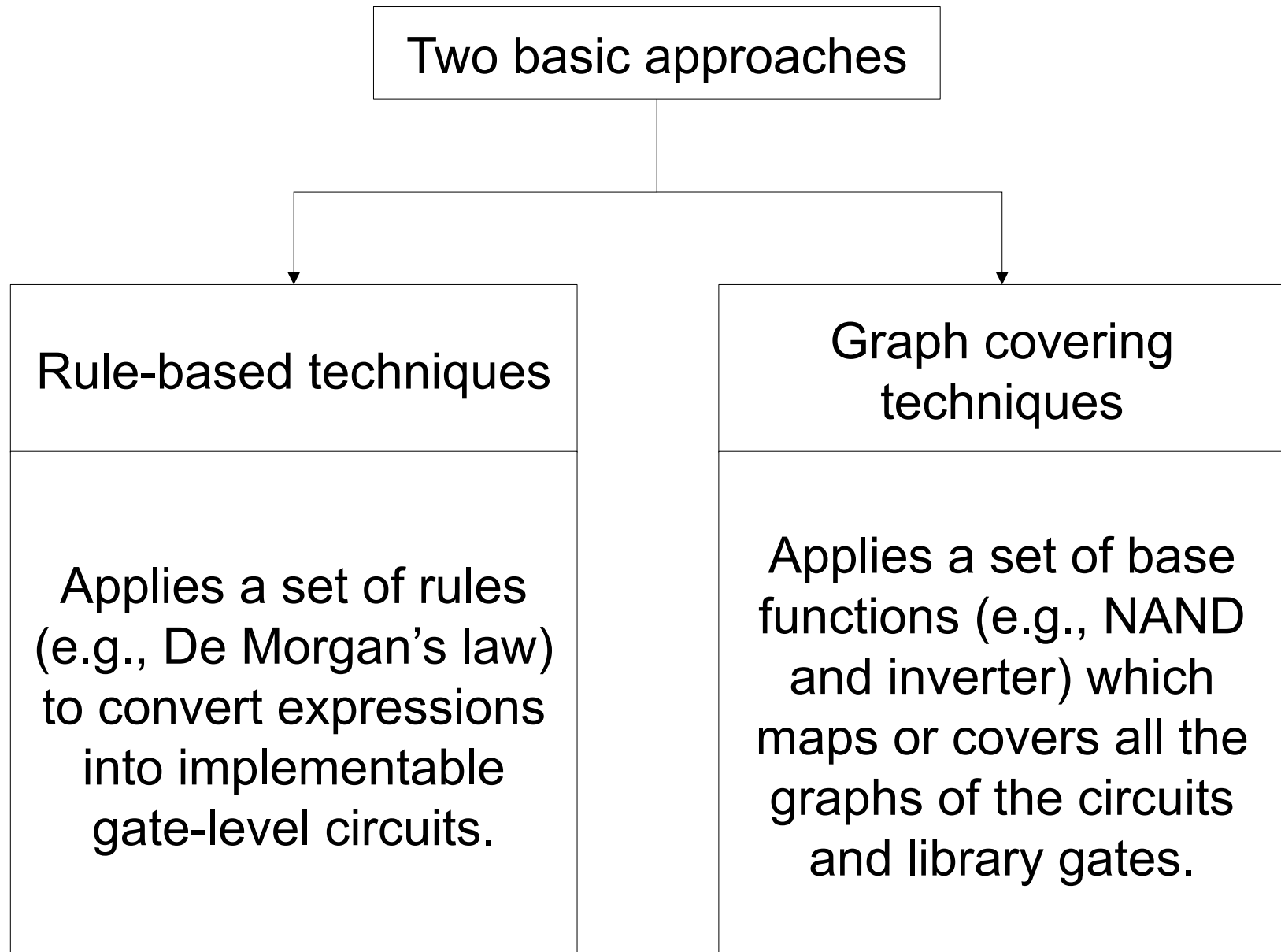
 
# Directed Acyclic Graph


- A graph made of nodes connected by directed edges.
- There are no cycles.
  - We can't start at a node and return to it by following the edges.
- In short, it is also called DAG.

A directed acyclic graph, where the circles are nodes and arrows are the directed edges.


 
# Logic Network in DAG Form

- If we consider the previous DAG example, and replace its nodes with various gates, inputs and outputs, we get:



So, combinational logic networks are basically DAGs!



# ***Prerequisites of the DAG-Covering Problem***

## Base Functions

- A set of chosen functions (e.g., a two-input NAND-gate and an inverter).
- Used to design the graphs of the logic function and the library gates.

## Subject Graph

- The simplified Boolean network is converted into the subject graph.
- Each node is restricted to one of the base functions.

## Pattern Graph

- The logic function for each library gate is converted into a pattern graph.
- Each node is restricted to one of the base functions.

# ***Goals of the DAG-Covering Problem***

- To find a “minimum cost covering” of the subject graph by choosing appropriate collection of pattern graphs.
- ↳ Covering means, every node of the subject graph is contained in one (or more) of the pattern graphs.
- ↳ Minimum cost covering means:
  - ⇒ Optimizing area of the cover.
  - ⇒ Optimizing minimum delay of the cover.

# Choice of Base Functions

- The choice is arbitrary as long as the base function set is functionally complete.
  - A functionally complete function can express any other function.
  - Such as, two-input NANDs and inverters.
- Different combinations of base functions produce different patterns of graphs.

$$f = (abcd + efgh + ijkl + mnop)'$$

- Base function set with:
  - Two-input, three-input, and four-input NAND-gates: 1 pattern.
  - Two-input NAND-gates and inverters: 18 patterns.

# ***Creating the Subject and Pattern Graphs***

- The logic function may have many combinations of graphs.
  - ↪ Happens due to the various possible combinations of the base function set.
- Each representation is a potential subject graph for DAG-covering.
  - ↪ Every one of these subject graphs (starting points) should be considered for an optimum covering.
- Similarly, many combinations of pattern graphs may also be generated.
  - ↪ Further increases the complexity of the DAG-covering problem.

# ***The DAG-Covering Problem Complexity***

- DAG-covering-by-DAGs is NP-hard!
  - ↳ NP-hard means it's not solvable in polynomial time.
  - ↳ Even with only three pattern graphs (inverter, two-input NAND, two-input NOR), and
  - ↳ Each subject graph node having no more than two incoming and outgoing edges.
  
- Heuristics can be a more effective approach.
  - ↳ But this is still an open problem.
  - ↳ L. Lavagno at U.C. Berkeley has achieved some degree of success.

# ***Alternative Approach: The Tree-Covering Problem***

- Reducing the DAG-covering problem to a set of tree-covering-by-trees problems.
  - ↪ Tree circuit is a single output circuit.
  - ↪ Each gate except the output, feeds exactly one other gate.
  - ↪ No fanout/branching at the outputs of any of the gates.


Partition the subject graph into trees  
by splitting it at the fanout points

Cover each tree optimally

Merge the tree-covers into a cover  
for the subject graph

 
# Splitting Subject Graph into Trees

- Let's consider the previous subject graph and split it:



The circuit on the left is not a tree, because there is one gate that feeds two other gates (marked as red crosses). So splitting it at these two locations, we obtained three trees (1, 2 and 3) on the right.

# ***The Tree Mapping Procedure***

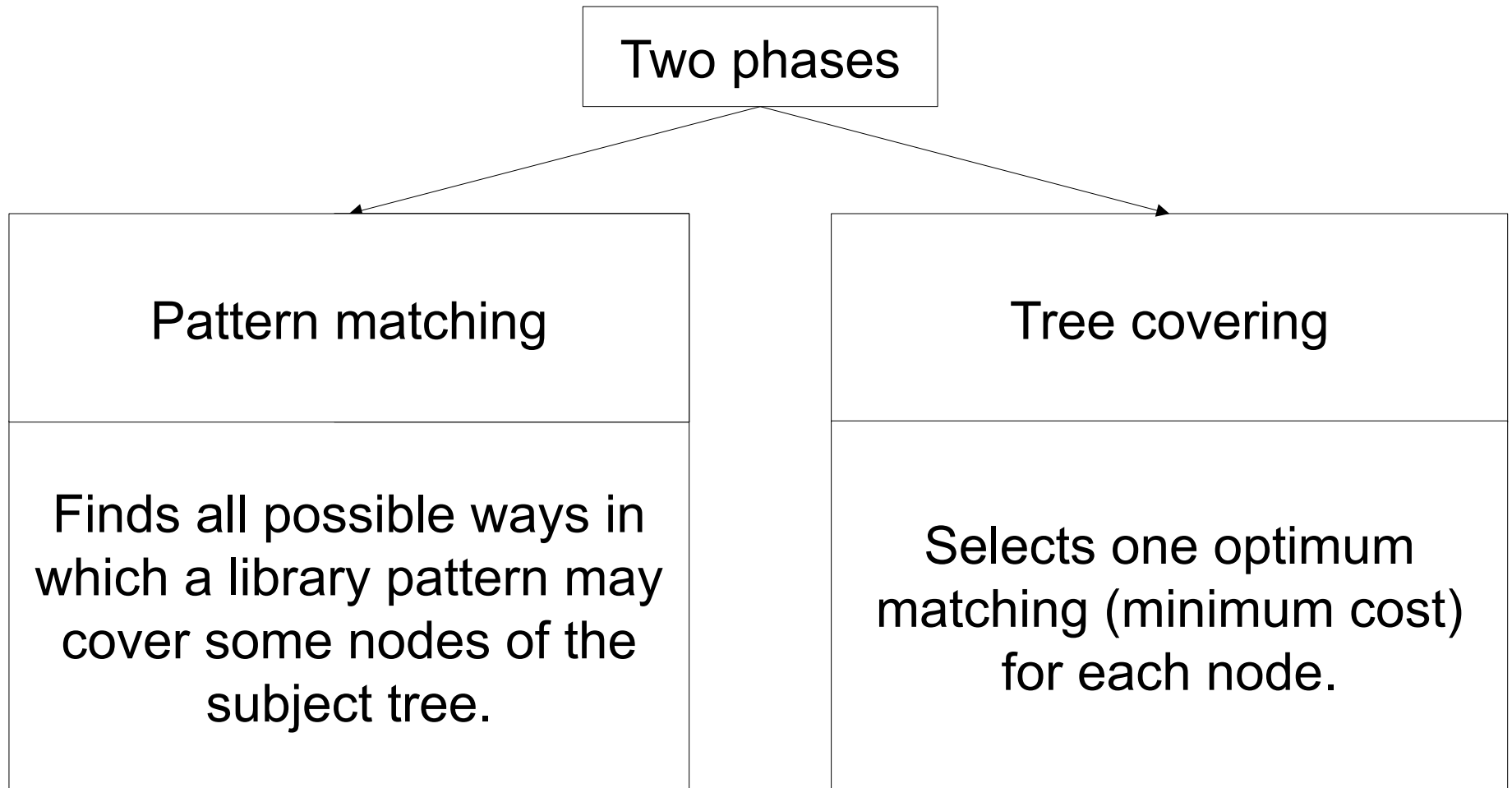



# Some Assumptions

- Let's consider the Tree-3 for pattern matching and the library containing three gates (INV,1; NAND2,2; NAND3,3) as shown below:

 


Figure: Tree-3 of the subject graph

 


Figure: Library gates

# Pattern Matching (Cover 1)

- If we select the three-input NAND gate to match the output node, then we cover gates f and g, besides h; hence, we do not need matches for f and g.

 


Figure: Tree-3 of the subject graph

 


Figure: Library gates

# Pattern Matching (Cover 2)

- If we choose the two-input NAND gate, then we need to select gates to cover *f* and *g*.

 


Figure: Tree-3 of the subject graph

 


Figure: Library gates

# Tree Covering (Cover 1)


 
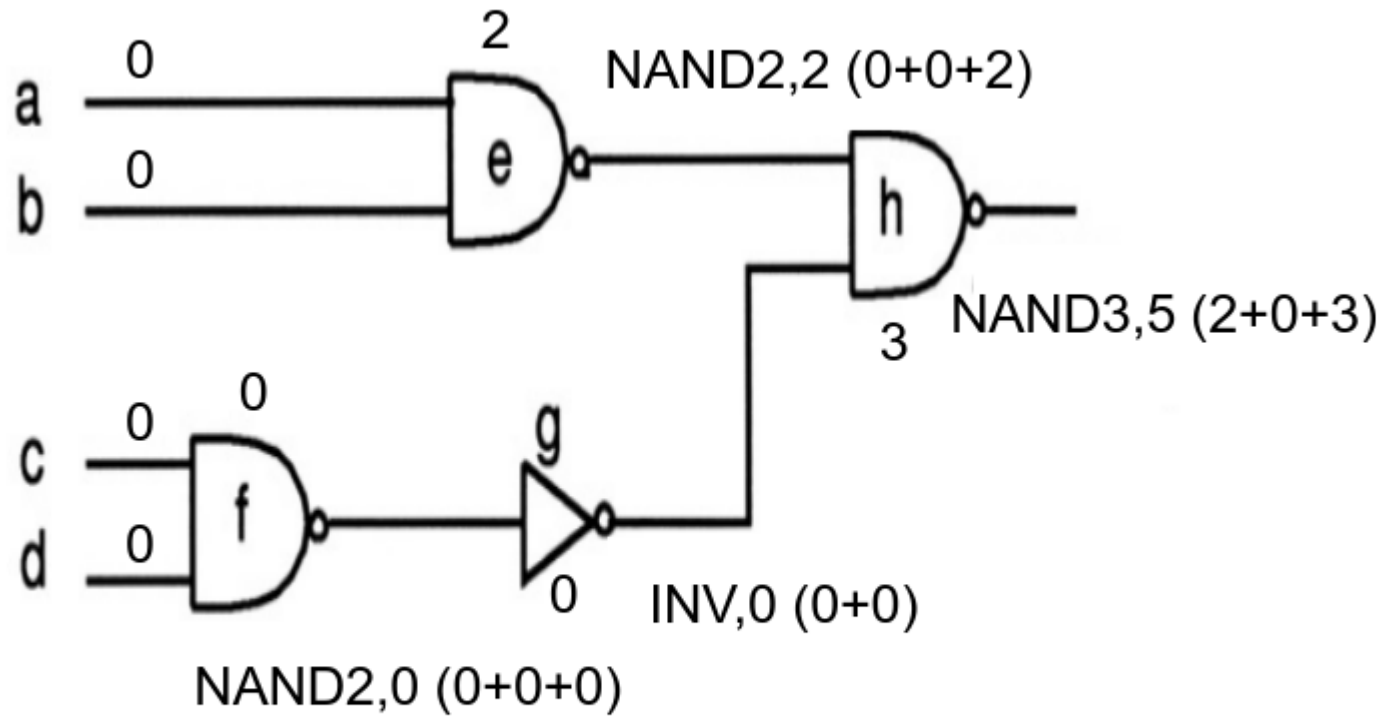


Figure: Optimum cover selection

 

# Tree Covering (Cover 2)


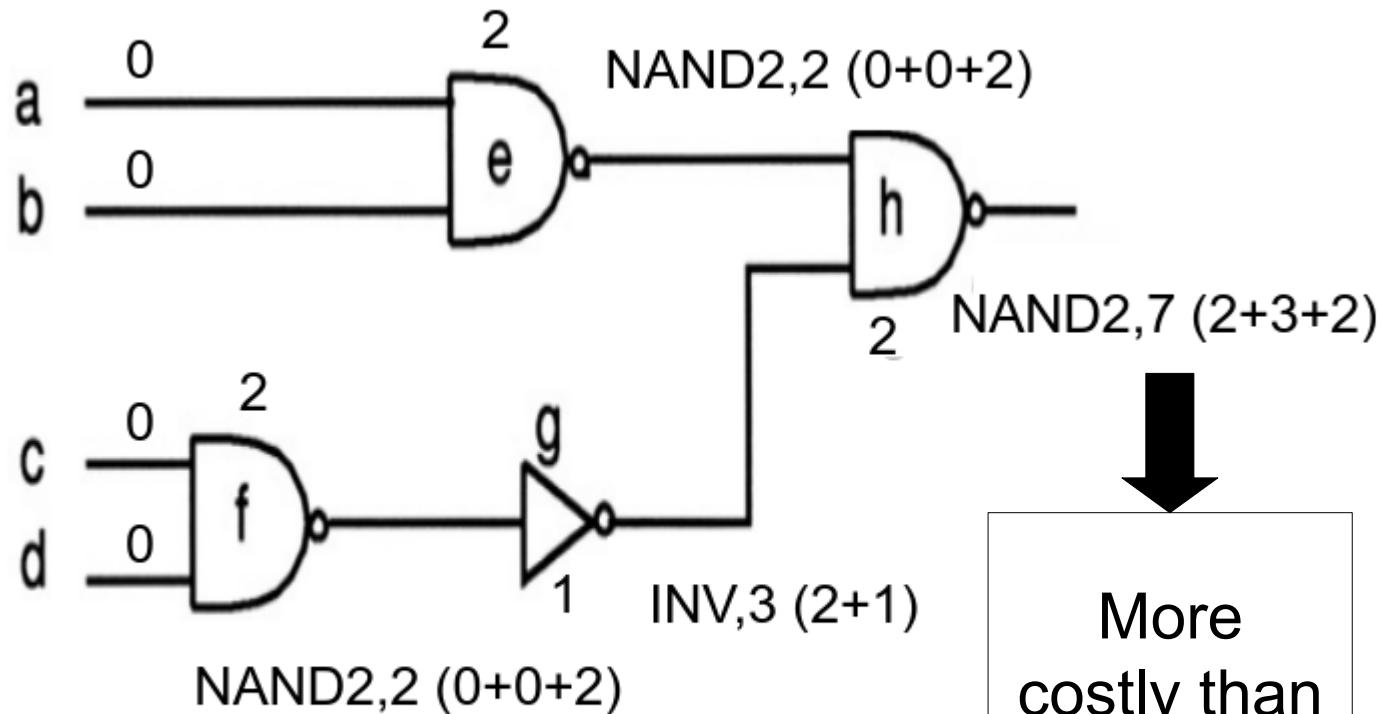
 


Figure: Optimum cover selection

 More costly than Cover 1, so it is discarded



# ***Advantages of Tree-Covering Problem***

- The NP-hardness of DAG-covering is removed.
- Linear complexity can be achieved due to splitting of the subject graph.
- Pattern matching is easier due to the reduction of search space.
- This method has proven to be quite effective.

# ***Limitations of Tree-Covering Problem***

- Loss of global view due to the step of partitioning into trees.
- Covers across partition boundaries are not allowed.
- Inefficient reduction of search space may affect the quality of the final solution.
- Does not always provide the exact optimum solution.

# ***References***

- Logic Synthesis and Verification Algorithms, Gary D. Hachtel and Fabio Somenzi.
- DAGON: Technology Binding and Local Optimization by DAG Matching, K. Keutzer.



***Thank You!***